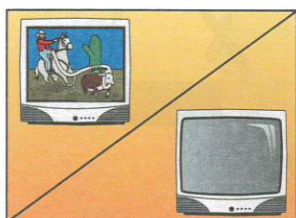


Electricity


Get **switched on** to this — it's a **powerful** section.

We get Electricity from the **Mains** or from **Batteries**


- 1) Many **appliances** (devices) in our homes use mains electricity to work. Without it our lives would be **darker**, **duller** and **colder**.




Televisions/Computers

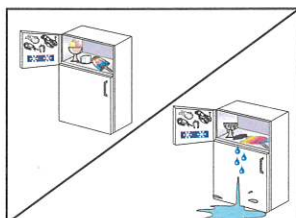

Fridges/Freezers

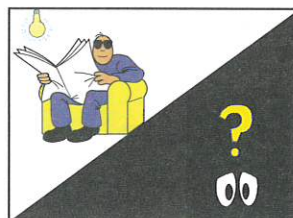


Lights

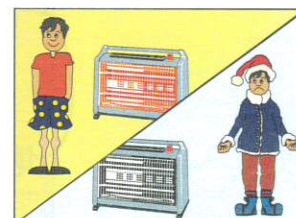

Heaters

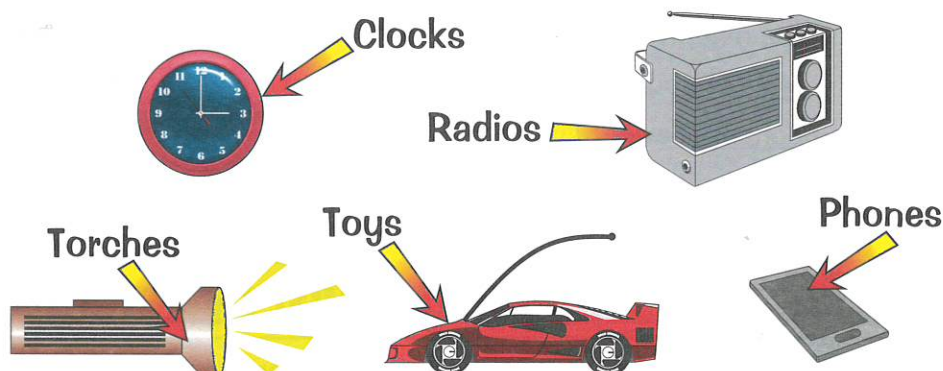- 2) Smaller electrical appliances often use **batteries** which store electricity. These appliances can be **moved** from place to place. Batteries eventually **run down** and need to be **replaced** or **recharged**. Batteries are sometimes called **cells**.



Electricity can be **Dangerous**

An electric shock from a mains socket **could kill you**. Electricity from the mains is a lot more powerful than electricity from a battery.

NEVER stick fingers, pens or anything else into a mains socket.

NEVER touch switches with wet hands.

NEVER use electrical appliances near water.

ALWAYS hold the plastic part of a plug when plugging in and unplugging appliances.





Safety Rules — **deadly serious...**

Think about all the things you use that run off **electricity** — it's amazingly useful. Without it we'd have no computers, no tellies, no mobile phones... But remember, you need to be **careful** when using electricity too — the **safety rules** aren't just for science lessons, they're for **everyday life**.

Circuits

Electricity can only Travel if there's a **Complete Circuit**

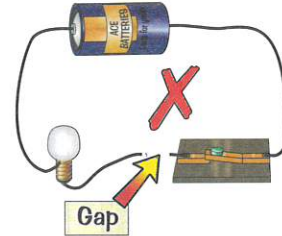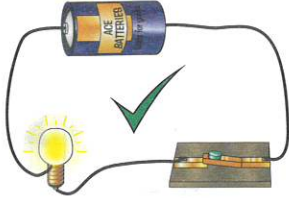
- 1) Electricity travels from the **power source**, such as a cell (battery), around a series of **conductors** (the circuit) **back** to the power source.
- 2) If there's a **gap** in the circuit **no** electricity will flow.



Simple Circuits can be set up using **Components**


Components are just things that can go in the circuit. An electrical circuit needs:

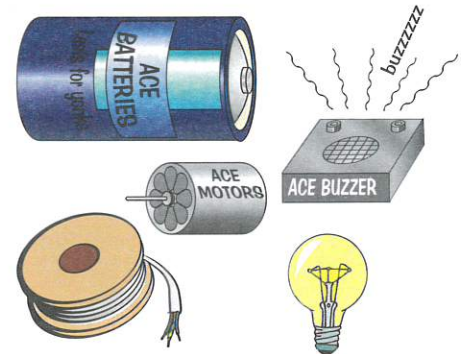- 1) A **cell (battery)** with wires connected to both the positive (+) and the negative (-) ends.
- 2) Wires made of **metal** (of course).
- 3) An electrical **component** (device) such as a bulb, a buzzer or a motor.




The Batteries and **Components** must be set up **Properly**

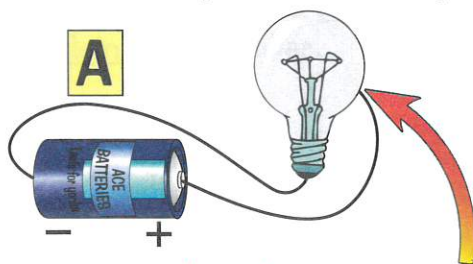
Batteries and components must be put together correctly for the circuit to work.



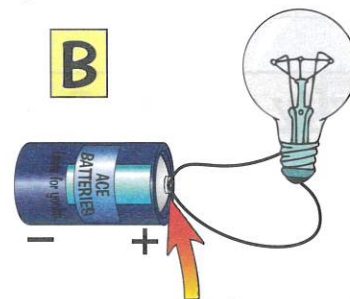
Circuit A **won't work** because the wire has been connected to the glass on the bulb (which is an insulator).



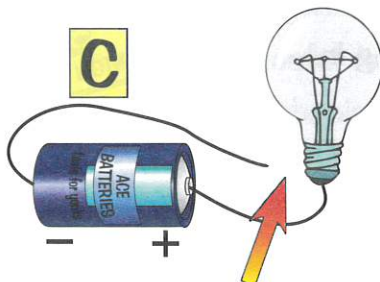Circuit B **won't work** because both wires are connected to the same end of the battery.



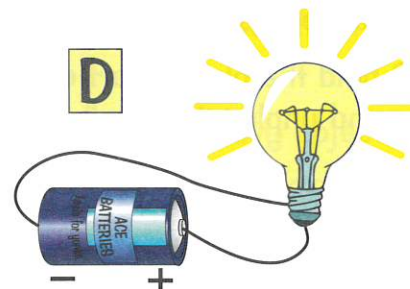Circuit C **won't work** because there is a gap in the circuit.

















HOORAY! Circuit D **will work** (as long as the battery isn't flat).


Circuit Diagrams

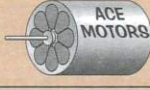Circuit Diagrams use **Symbols** instead of **Pictures**

Make sure you know these symbols, and use them when you're drawing circuit diagrams:

Component	Picture	Symbol
Cell (battery)		
Two cells (batteries)		
Bulb		
Buzzer		
Motor		
Switch (off)		
Switch (on)		

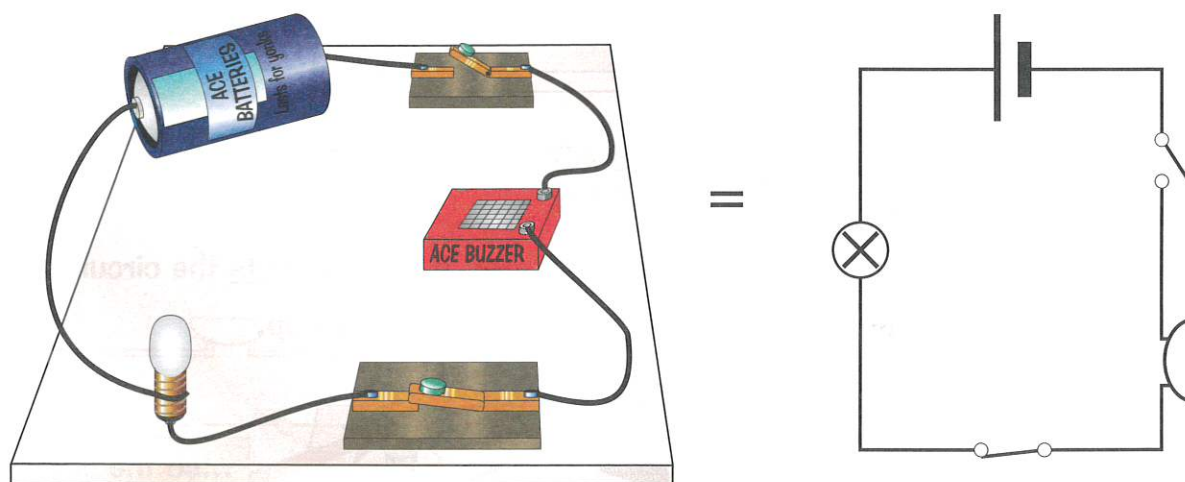Here's a circuit diagram showing a cell (battery), two switches, a bulb and a buzzer:



Use symbols in circuits — but do it quietly...

This electricity stuff does look a bit complicated, but if you remember the **basic facts** on these pages, you should be sorted. Electricity has to get from one end of the battery back to the other end of the battery for the circuit to work — no electricity will flow if there's a gap in the circuit. Circuit diagrams use symbols as a kind of shorthand, so get stuck in and **learn** all the symbols.

Conductors and Insulators

Materials are Either **Conductors** or **Insulators**


- 1) Electrical conductors **allow** electricity to pass through them.
- 2) **Metals** are good conductors of electricity.
- 3) Electrical **insulators** do **not** allow electricity to pass through them.
- 4) **Wood, plastic, glass** and **rubber** are all electrical insulators.

You Can **Test** a Material to see if it's a **Conductor**

To find out if a material conducts electricity, you can make a circuit using a **battery**, a **bulb**, some **wires** and a piece of the **material**.


TESTING AN INSULATOR:

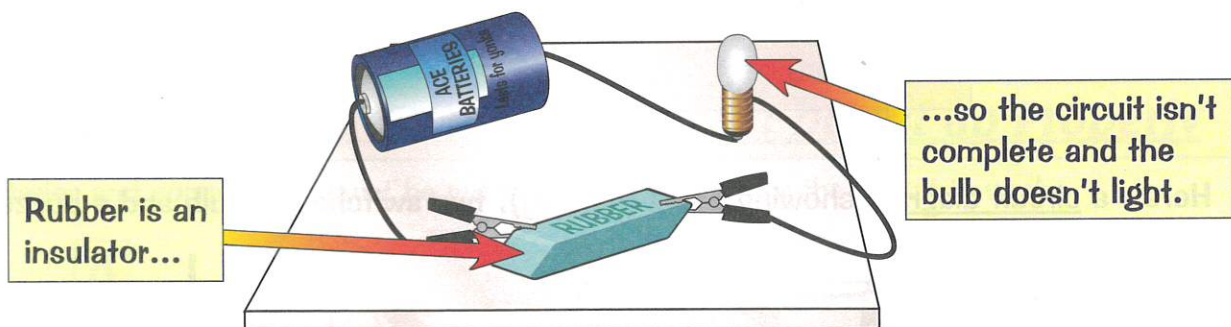- 1) Electricity can only travel around a **complete** circuit of **conducting** components.
- 2) If the material that you're testing is an **insulator**, the bulb **won't** light up because electricity can't flow around the circuit.



TESTING A CONDUCTOR:

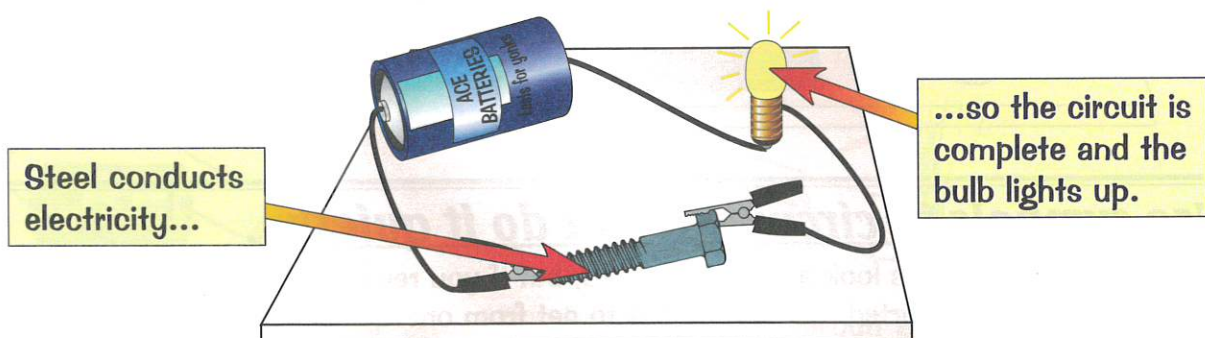- 1) If the material that you're testing is a **conductor**, it will **complete** the circuit.
- 2) Electricity will flow around the circuit and the bulb **will** light up.




Switches


You know how to make circuits — well you can use **switches** to control where the **electricity** goes and where it **doesn't**.

Switches Control the Flow of Electricity in a Circuit

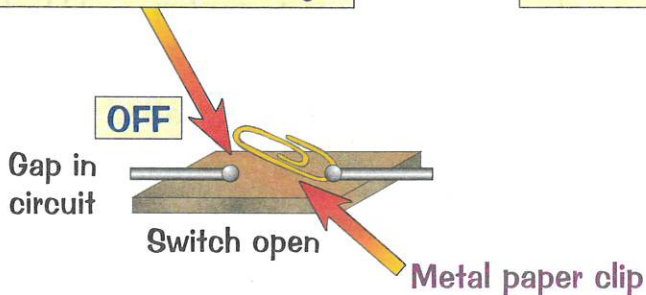1) Making a gap stops the flow of electricity.




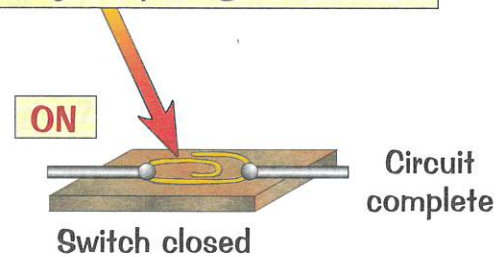2) Closing the gap allows electricity to flow by completing the circuit.




Switches Control Part of a Circuit

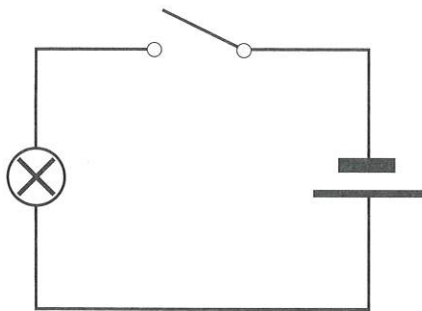
Take a look at the switches in these circuit diagrams — some are **open** and some are **closed**. See if you can work out if the bulbs will **light** or the buzzers will **sound**.



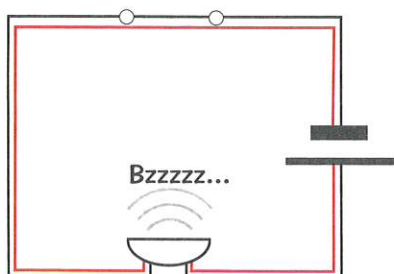The switch is **open** so no current will flow. The bulb will **NOT** light.



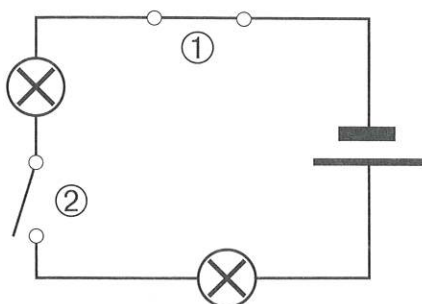The switch is **closed**, so current can flow, and the buzzer **sounds**. The **red** line shows the route the electricity takes.




Switch ① is **closed**, but switch ② is **open**. **Neither** bulb lights because current cannot flow around the entire circuit.

Changing Circuits

Now it's time to look at some very slightly more complicated circuits — don't panic. You're just taking a simple circuit (battery, switch, wires and bulb) and altering the components.

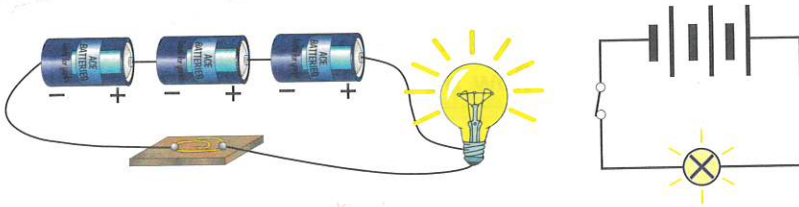Add More Batteries — the bulb gets **Brighter**




(If this circuit had a buzzer instead, it would be louder than with just one battery.)

THE MORE BATTERIES — THE BRIGHTER THE BULB

Be careful though — too many batteries will destroy the bulb.

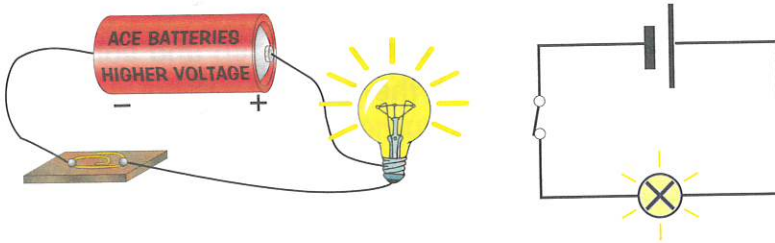Use Higher Voltage Batteries — the bulb gets **Brighter**




The higher the voltage of a battery, the more powerful it is.

(Using a higher voltage battery would also make a buzzer louder.)

THE HIGHER THE VOLTAGE OF THE BATTERIES — THE BRIGHTER THE BULB

Again, be careful though — using a very high voltage will destroy the bulb.

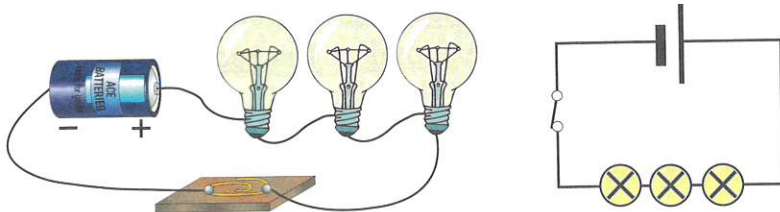Add More Bulbs — the bulbs get **Dimmer**



(Several buzzers would each buzz more quietly than just one.)

Several motors would each turn more slowly than just one.)

THE MORE BULBS — THE DIMMER THE LIGHT




Add more Science to your life — you'll get brighter...

This stuff isn't too bad if you think it through. If you want to make a bulb brighter, you need to give it more power. That means using more batteries or higher voltage batteries. Adding more bulbs to a circuit means that each bulb gets less power, so they all get dimmer. The same ideas apply to all components — lamps change brightness, buzzers change volume and motors change speed.

Summary Questions for Section Nine

Electricity may seem like a tough topic but it's not nearly as bad as it looks. It's the circuit diagrams that make it seem frightening — but **remember** the diagrams are just an **easier** way to draw a **picture** of the real circuit. **Practise** drawing circuit diagrams containing **switches**, **batteries** and different **components**. Remember that the idea is to keep on bashing away at these questions until you can do **all** of them. If one or two look a bit tricky **don't** leave them out — go back and look through the section again, and **keep trying**. Ready? Three, two, one, GO...

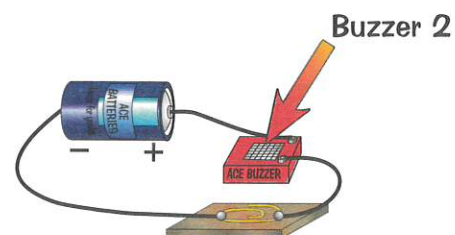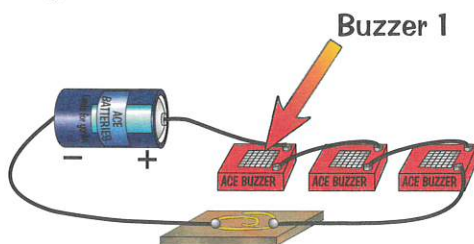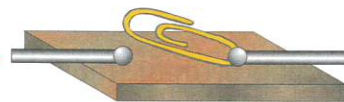- 1) Name **four** things in your house that **wouldn't work** without **mains electricity**.
- 2) Why is it better for some appliances to use **batteries**?
- 3) Why must you **not** push things (other than plugs) into mains sockets?
- 4) What happens when a circuit has a **break** (or gap) in it?
- 5) Imagine you are making a **circuit**. Should you connect **one wire** to **each end** of the battery, or **two wires** to **one end** of the battery?
- 6) Name **three** electrical components used in simple circuits.
- 7) Imagine that someone has made a simple circuit using a battery, wires and a bulb. The bulb doesn't light up. Give **three** reasons to explain what might be wrong.
- 8) Draw a **circuit diagram** showing a circuit with: a cell (battery), wires, an open switch and a bulb
- 9) Draw a **circuit diagram** showing a circuit with: two cells (batteries), wires, an open switch and a buzzer.
- 10) What is a material that **doesn't** conduct electricity called?
- 11) Why are electrical **wires** made of metal?
- 12) Why is there usually a **plastic** coating around a metal wire?
- 13) How could you **test** a material to see if it conducts electricity?
- 14) How does a simple **switch** work?
- 15) Is the switch on the right **ON** or **OFF**?
- 16) How could you make a bulb in a circuit **brighter**?
- 17) Look at the two circuits below. Which will be **louder** — Buzzer 1 or Buzzer 2? Explain your answer.



The answers to these questions are on pages 101-102.